## IZMIR KATIP CELEBI UNIVERSITY DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING EEE458 MICROELECTRONIC CIRCUITS MID-TERM EXAM OF 2019-2020 SPRING



## Design an FPGA-based circuit using VHDL to satisfy following rules:

- \* There is one LED. Normally, it gives no light.
- \* There are three buttons: Player1, Player2, and StartStop.
- \* There are three switches to encode the time: **000**: 1 minute, **001**: 3 minutes, **010**: 5 minutes, **011**: 10 minutes, **100**: 15 minutes, **101**: 30 minutes, **111**: 90 minutes.
- \* There are two switches to encode the additional time: 00: 0 seconds, 01: 2 seconds, 10: 3 seconds, 11: 5 seconds.
- \* There are two displays where 4 digits for each. Each display shows the remaining time in minutes (2 digits) and seconds (2 digits) for the corresponding player.
- \* When the button of StartStop is pressed, the device will start if it is stopped (and both timers will stop), or the device will stop if it is started.
- \* When the device is started as the first time, the time of the Player1 will start to decrease.
- \* When the button of Player1 is pressed, the time of the Player1 is stopped but the time of the Player2 will start to decrease.
- \* When the button of Player2 is pressed, the time of the Player2 is stopped but the time of the Player1 will start to decrease.
- \* If one of the timers reaches the zero, then buttons of Player1 and Player2 will not work anymore. In addition, the LED will give light.
- \* When the button of Player1 is pressed, the timer of the Player1 will increase by the pre-configured additional time.
- \* When the button of Player2 is pressed, similarly, the timer of the Player2 will increase by the pre-configured additional time.
- \* Use the system clock as 50 MHz.
- \* You should implement the module itself with a separate top module, simulate your answer as a video. Finally, please upload your answer as a single zip file including VHDL codes and the video file until 23:59 on June 10, 2020. (3)